

# CME 341: Synchronous Logic, Part 2

Brian Berscheid

Department of Electrical and Computer Engineering  
University of Saskatchewan



# Today's agenda

## 1 Basic features of flip-flops



## Basic features of flip-flops

# Flip-flops

- Flip-flops (FFs) are the key element of synchronous logic
- There are many different types of FFs; the most commonly used type in FPGAs is the D-FF (introduced last time)
- Focusing on D-FFs, there are a number of sub-types which have various input-output and timing relationships
- This section introduces the D-FF sub-types and investigates their behavioral Verilog descriptions
  - ▷ Clear/Reset functionality (asynchronous or synchronous)
  - ▷ Set/Preset functionality (asynchronous or synchronous)
  - ▷ Data load functionality (asynchronous or synchronous)

# D-FF with asynchronous clear

  Example shows active low, but could also be active high.



“When a negative edge of the clear signal occurs, immediately reset Q to 0.  
If a clock edge occurs while clear is active, hold Q at 0.  
Otherwise, set Q to D when the clock arrives.”

# D-FF with asynchronous clear - Verilog description



## Translating description of operation into code

“When a negative edge of the clear signal occurs, immediately reset Q to 0.  
If a clock edge occurs while clear is active, hold Q at 0.  
Otherwise, set Q to D when the clock arrives.”

```
reg q;  
  
always @ (posedge clk or negedge clr_n)  
    if (clr_n == 1'b0)  
        q = 1'b0;  
    else  
        q = d;
```

# D-FF with synchronous clear

  Example shows active low, but could also be active high.



“When a positive edge of the clock signal occurs, check if clear is active. If so, set Q to 0. Otherwise, set Q to D.”

# D-FF with synchronous clear - Verilog description

Translating description of operation into code

“When a positive edge of the clock signal occurs, check if clear is active.  
If so, set Q to 0. Otherwise, set Q to D.”



```
reg q;

always @ (posedge clk)
  if (clr_n == 1'b0)
    q = 1'b0;
  else
    q = d;
```


  
# D-FF with asynchronous preset

Similar to clear, but sets FF output to 1



“When a negative edge of the preset signal occurs, immediately set Q to 1.  
If a clock edge occurs while preset is active, hold Q at 1.  
Otherwise, set Q to D when the clock arrives.”

# D-FF with asynchronous preset - Verilog description

Translating description of operation into code

“When a negative edge of the preset signal occurs, immediately set Q to 1.  
If a clock edge occurs while preset is active, hold Q at 1.  
Otherwise, set Q to D when the clock arrives.”



```
reg q;

always @ (posedge clk or negedge pre_n)
  if (pre_n == 1'b0)
    q = 1'b1;
  else
    q = d;
```

Try to sketch the timing diagram and hardware for a D-FF with synchronous preset.  
Then write the corresponding Verilog code.

# D-FF with synchronous preset

  Example shows active low, but could also be active high.



“When a positive edge of the clock signal occurs, check if preset is active.  
If so, set Q to 1. Otherwise, set Q to D.”

## D-FF with synchronous preset - Verilog description

“When a positive edge of the clock signal occurs, check if preset is active.  
If so, set Q to 1. Otherwise, set Q to D.”

```
reg q;

always @ (posedge clk)
  if (pre_n == 1'b0)
    q = 1'b1;
  else
    q = d;
```

## Key observations

- When an asynchronous clear or preset is used, the corresponding signal must be added to the sensitivity list with a 'posedge' or 'negedge' designation.
  - ▷ Must be accompanied by a test in the procedure body:  
Test for signal == 1 if posedge  
Test for signal == 0 if negedge
- The FF primitive used in CME 341 (DFFE) includes asynchronous active low preset and clear ports
- Synchronous clear and preset are achieved by placing additional logic in front of the FF to control its D input

## Example: D-FF with asynchronous preset and asynchronous clear

```
reg q;  
always @ (posedge clk or negedge pre_n or negedge clr_n)  
    if (clr_n == 1'b0)        // clear overrides set in this example  
        q = 1'b0;  
    else if (pre_n == 1'b0)  
        q = 1'b1;  
    else  
        q = d;
```


Note: Just an example of the behavior description process...  
It is not usually necessary to have both asynchronous preset and clear.

# Asynchronous load

Load an input signal rather than a constant

```
reg q;

 always @ (posedge clk or posedge load)
  if (load == 1'b1)
    q = load_val; // load_val is a variable
  else
    q = d;
```





### Challenge:

Write a Verilog module which implements an 8-bit counter that is asynchronously preloadable and has a count enable.

Solution in video...

## A FF with two clocks?

- Suppose you write the following Verilog code:

```
reg q;
```


```
always @ (posedge clk_1 or posedge clk_2)
```

```
    q = d;
```

- Two posedges in sensitivity list, neither being used as async preset/clear
- Intention is to copy d into q whenever a posedge of either clk\_1 or clk\_2 occurs
- What hardware is built?
 
# A FF with two clocks - common misunderstanding

Can't OR the two clocks together... clock edges will be missed



This circuit does not work as intended.  
It is not possible to build a FF with two clocks using FPGA technology!

Thank you!  
Have a great day!