

CME 341: Block Diagrams, Primitives, and Assignments

Brian Berscheid

Department of Electrical and Computer Engineering
University of Saskatchewan



Today's agenda

- 1 Interpreting Block Diagrams
- 2 Building Logic with Verilog: Explicit Structural Method
- 3 Building Logic with Verilog: Implicit Structural Method

Interpreting Block Diagrams

Module Instantiations: Review

- A module can be instantiated inside another module
- The module prototype is like a blueprint or template that is used by Verilog to create objects (instances)
- Each instantiated module needs a unique instance name
- Need to connect signals (generally wires) to the ports of the instance
 - ▷ Signals should be declared before they are connected
 - ▷ Much more on signal types later...
- The hierarchy can be nested as deeply or as shallowly as you like

Goto Chapter 1 Notes, Pages 9-13 on Block Diagrams

Declaring Signals

- Signals must be declared before they are used
- There are two main data types of interest in CME 341: reg and wire
- For now, stick with wire (reg will be discussed in detail later)
- To declare a signal, just use:

```
wire my_wire_name; // declares a 1-bit wire  
reg  my_reg_name;  // declares a 1-bit reg
```
- Note that Verilog is case sensitive!


Vectors

- It is convenient to declare multi-bit signals (“vectors”) to represent data buses
- To do so, just specify the bit width in the signal declaration:

```
wire [3:0] my_wire_name; // declares a 4-bit wire
reg [7:0] my_reg_name; // declares an 8-bit reg
```
- Any time the name of a vector is used, it refers to the full set of bits
- Can access individual bits, ie. `my_wire_name[3]` // MSB of vector
- The notation `[3:0]` indicates that bit `[3]` of the vector is the MSB and bit `[0]` is the LSB
- It is possible to define vectors in the opposite orientation (with bit `[0]` as the MSB) as below, but this is **very strongly discouraged**

```
wire [0:3] my_wire_name; // DON'T DO THIS !!!
```

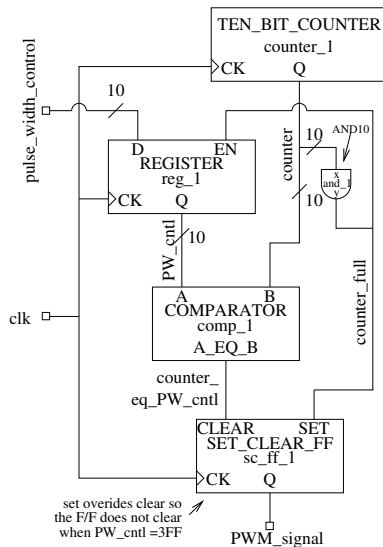Challenge: Write the Verilog to Represent this PWM Diagram



Building Logic with Verilog: Explicit Structural Method

Logic Construction Approaches

- There are three main methods of building logic inside a module:
 - ▷ Explicit structural approach: manually instantiating and wiring primitives
 - ▷ Implicit structural approach: using operators to implicitly instantiate primitives
 - ▷ Behavioral approach: describing the behavior of the circuit under certain conditions
- The list above goes from lower to higher levels of abstraction (and ease of use)
- It is possible (and common) to mix these approaches within a module
- Behavioral methods will be discussed in detail in Chapter 3; for now we will focus on the structural approaches




Verilog Built-In Primitives

- Verilog has a set of built-in logic primitives that can be directly instantiated in your code
- The most used primitives correspond to the basic logic gates studied in EE 232:
`and`, `nand`, `or`, `nor`, `xor`, `xnor`, `not`
- All (except for `not`) accept a variable number of 1-bit inputs and produce a 1-bit output
- `not` accepts a single 1-bit input and produces a 1-bit output
- Generally need to handle individual bits of vectors separately
- As always, instances of primitives require unique instance names
- The port names are omitted in primitive instantiations
 - ▷ Output port comes first


Primitive Instantiation Examples:

```
// declare signals
wire in_wire_1, in_wire_2, in_wire_3;
wire out_wire_1, out_wire_2, out_wire_3;

   // instantiate primitives
and and_1 (out_wire_1, in_wire_1, in_wire_2);
nor my_nor (out_wire_2, in_wire_1, in_wire_2, in_wire_3);
not any_name_you_like (out_wire_3, in_wire_3);
```



 Challenge: Write Explicit Structural Verilog to Implement this Comparator



Building Logic with Verilog: Implicit Structural Method

The assign statement

- Implicit structural logic is constructed using the assign statement as follows:
`assign target_wire = expression;`
- `target_wire` (LHS of statement) can be any wire or vector you have previously declared
- The expression (RHS of statement) is built by combining signals and operators
- Can cascade multiple operators to build complex expressions
(use parentheses to make order of operations clear)
- If vectors are used, the operations and assignment are performed on a per-bit basis (sizes MUST¹ match)

¹Technically not a MUST, but doing otherwise is DANGEROUS and DISCOURAGED. This will be discussed in more detail later in the course.

Operators used with assign

- There are two ways operators can be used:
 - ▷ Bitwise operation: requires two operands, performs bitwise operation between corresponding bits of operands
 - ▷ Reduction operation: requires one operand, performs operation between all bits of operand (single-bit output)
- Not all operands can be used in both modes

<code>~</code>	inverter / not (one operand; bitwise negation)
<code>&</code>	and (bitwise or reduction)
<code>~&</code>	nand (reduction only)
<code> </code>	or (bitwise or reduction)
<code>~ </code>	nor (reduction only)
<code>^</code>	xor (bitwise or reduction)
<code>^^</code>	xnor (bitwise or reduction)


assign statement examples

```
// declare signals
wire in_wire_1, in_wire_2, in_wire_3;
wire [3:0] vec_1, vec_2, vec_3;
wire out_wire_1, out_wire_2, out_wire_3, out_wire_4;

// instantiate primitives
// examples from primitive section
assign out_wire_1 = (in_wire_1 & in_wire_2);
assign out_wire_2 = ~(in_wire_1 | in_wire_2 | in_wire_3);
assign out_wire_3 = ~in_wire_3;

// vector examples
assign vec_3 = (vec_1 & vec_2); // bitwise AND
assign out_wire_4 = & vec_1;    // reduction operator, single bit output
```

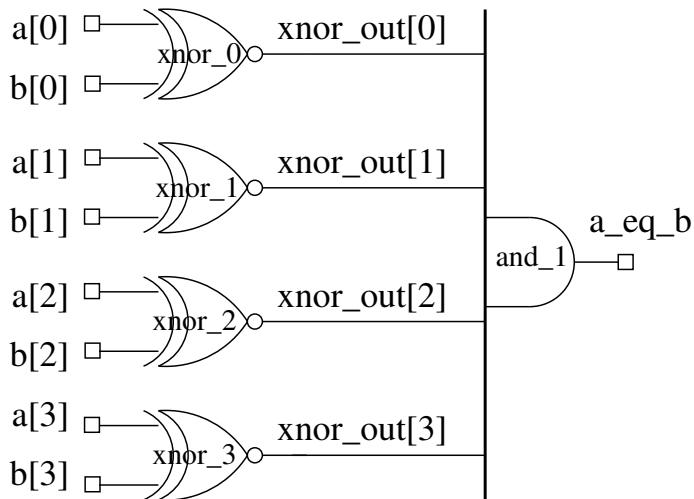Challenge: Write Implicit Structural Verilog to Implement this Comparator



Thank you!
Have a great day!