

# CME 341: Introduction to Behavioral Verilog

Brian Berscheid

Department of Electrical and Computer Engineering  
University of Saskatchewan



# Today's agenda

- 1 Introduction to Behavioral Verilog
- 2 If-else statement
- 3 Case statement

# Introduction to Behavioral Verilog

# Behavioral coding

- Alternative to structural coding: specify the *behavior* of the circuit
  - ▷ How does the behavior of the output signals depend on the input signals?
- Synthesizer translates description of behavior into individual gates + connections
- Very powerful; can represent large amount of logic with small amount of code
- We need to follow certain conventions to ensure the translation is done as intended
  - ▷ It is important to keep in mind how the synthesizer works and not just treat Verilog as a sequential programming language (like C, python, etc.)

# Procedures

- Behavioral logic is built within *procedures*: blocks of code which specify two things
  - ▷ When to execute
  - ▷ What to do when executing
- In CME 341, we will study two main types of procedures:
  - ▷ `initial`: executes once at start of simulation (not normally synthesizable)
  - ▷ `always`: executes every time a certain condition is met
- `initial` procedures have already been seen in an example testbench
- Most of our efforts in CME 341 will be focused on `always` procedures

## Procedures: key facts to remember

- Any variables being modified within a procedure must be defined as type `reg`, not `wire`!
  - ▷ Confusingly, type `reg` doesn't necessarily build a register in hardware; it is just a data type that allows behavioral assignment!
- Procedures are one statement long by default
  - ▷ Can include multiple statements if wrapped in `begin ... end`
- To set a variable to some expression, just use:  
`variable = expression; // ‘assign’ not needed (or allowed)`
- Verilog is a parallel language... procedures run in parallel!

## Recall: examples of initial procedures in testbench code

```
reg n_set, n_clear; // define registers

initial // runs once at simulation startup
begin
#10 n_set = 1'b0;    // schedule n_set to be 0 at t=10 ns
#10 n_set = 1'b1;    // schedule n_set to be 1 at t=10+10=20 ns
#55 n_set = 1'b1;    // schedule n_set to be 1 at t=20+55=75 ns
end

initial
#65 n_set = 1'b0;    // schedule n_set to be 0 at t=65 ns
```

# Syntax of an always procedure

```
always @ (sensitivity_list)  
    statement;
```

// OR

```
always @ (sensitivity_list)  
    begin  
        statement_1;  
        statement_2;  
        // etc...  
    end
```

- Sensitivity list defines “when to do it?”

- Statement(s) define “what to do?”




# Combinational vs synchronous<sup>1</sup> logic

- always procedures can be used to build combinational or synchronous logic
- Synchronous: happening at the same time (from ancient Greek)
  - ▷ Refers to logic that operates based on a clock signal (typically at the positive edge)
  - ▷ Key element is a “flip-flop” or “register”: passes signal from input to output on clock
- Combinational: logic which creates outputs based on combinations of inputs
  - ▷ No notion of time or clock signal involved
  - ▷ Standard logic gates: AND, OR, NAND, NOR, etc.
- Note that synchronous logic generally combines flip-flops with combinational logic gates


---

<sup>1</sup>Also known as sequential logic

# Combinational vs synchronous logic

 

Combinational Logic

 

Synchronous Logic


## Sensitivity lists for combinational vs synchronous logic

- The sensitivity list defines whether an `always` block generates synchronous or combinational logic
  - ▷ Combinational logic: has form `always @ (a or b or c)` or `always @ (*)`
    - Means “run procedure whenever a or b or c changes”
    - \* is a shortcut which automatically creates a sensitivity list containing all signals on RHS of assignments (strongly recommended)
  - ▷ Synchronous logic: has form `always @ (posedge clk)`
    - Means “run procedure whenever a positive edge of clk occurs”
- We will study both types in CME 341, but will start with combinational logic
  - ▷ Many common rules and principles apply to both types

# Example: combinational vs synchronous logic

```
always @ (*)
```


```
    E = (A & B & C & D);
```

 

Combinational Logic


```
always @ (posedge Clk)
```

```
    E = (A & B & C & D);
```

 

Synchronous Logic

# Summary: taxonomy of procedures

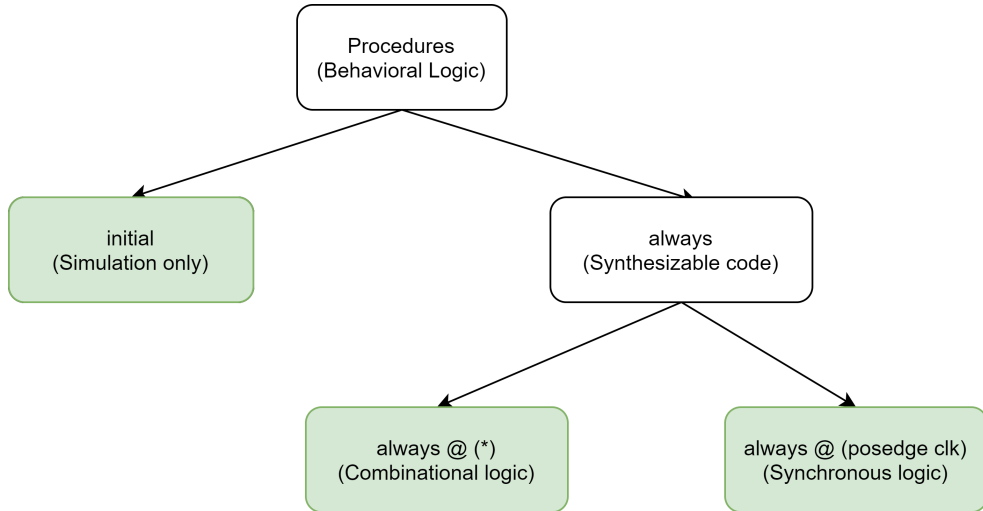

# Synthesis templates

- Synthesizer parses the Verilog code looking for structures that match *templates*
  - ▷ Template: a specific coding structure that maps to hardware in a predictable way
- Templates are where the power of behavioral coding really becomes evident
- Understanding how code maps into hardware through templates is critical to digital design
- We will study two of the most important templates / coding constructs in the following sections:
  - ▷ `if ... else`
  - ▷ `case`

## If-else statement

## If-else statement: basics

- Represents hardware which takes one of two actions depending on the result of a test
- Similar structure to many programming languages, but don't forget that it is building hardware!
- Syntax:

```
always @ (*)  
    if (conditional_test)    // no semicolon  
        statement_if_true;  
    else                    // no semicolon  
        statement_if_false;
```


- Conditional test can be anything that evaluates to a single-bit (boolean) value:
  - ▷ Review operators section if necessary
  - ▷ Reduction operators and relational operators are commonly used here



# If-else statement: example 1

```
reg C;  
  
always @ (*) // equivalent to (A or B or C or D)  
  if (A == B)  
    C = D;  
  else  
    C = E;
```
 
# If-else statement: hardware for example 1




## Nesting of if-else

- if-else statements can be nested to represent more complex logic
- Place another if statement in the else condition as shown below... can nest as deep as desired

```
always @ (*)  
  if(Test_1)  
    Out = A;  
  else if(Test_2)  
    Out = B;  
  else if(Test_3)  
    Out = C;  
  else  
    Out = D;
```

# Hardware for nested if-else

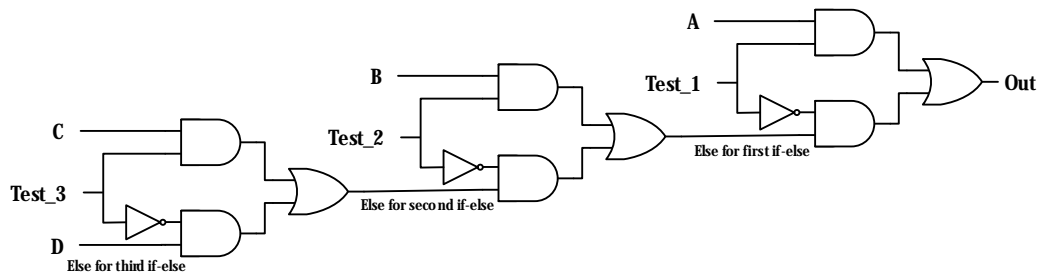

# Challenge

Try to write a Verilog module to solve the following problem

Generate a circuit which analyzes an 8-bit input value called `price` and generates a 2-bit output called `flag` whose value is chosen based on the value of `price`.

If the `price` is odd and greater than 13, `flag` should be set to 2. If the `price` is even, `flag` should be set to 0. Otherwise, `flag` should be set to 1.

## Danger: latch warning!

- When writing if-else conditions, make sure all cases are covered (make sure you have an else for each statement)
  - ▷ It is legal but dangerous to omit the else, especially in a combinational circuit
  - ▷ If you omit the else, the compiler will add one for you which leaves the values at their previous states
  - ▷ This adds feedback to the circuit and risks creating a latch (if circuit is combinational)
  - ▷ Recall from previous discussions that latches can behave unpredictably and even go unstable
  - ▷ Quartus will produce a warning if this happens
- This is a **VERY COMMON** source of errors for people new to Verilog!

# Inferred latch example


Suppose you write the following code:

```
always @ (*)  
  if (A == B)  
    C = D;
```
 
# Inferred latch example

Compiler adds else case

```
always @ (*)  
if (A == B)  
    C = D;  
else  
    C = C;
```





## Case statement



# What is a case statement?

- A case statement analyzes an input vector and take one of multiple actions depending on the value of the input
- Like the if-else statement, it must reside within a procedure (combinational or synchronous)
- Similar to the if-else construct in functionality, but allows for more than 2 possibilities
- Synthesizes to an N-to-1 multiplexer hardware structure or “multi-throw switch”

## Case statement example

```
module data_selector (  
    input wire data_in_0, data_in_1, data_in_2, data_in_3,  
    input wire [1:0] s,  
    output reg data_out  
);  
  
always @ *  
    case(s)  
        2'b00: data_out = data_in_0;  
        2'b01: data_out = data_in_1;  
        2'b10: data_out = data_in_2;  
        2'b11: data_out = data_in_3;  
    endcase  
endmodule
```
  
# Hardware representation of case statement





# General case statement syntax

```
case (select_expression)
  alternative_1: statement_1;
  alternative_2: statement_2;
  // etc...
  default: statement_default;
endcase
```

Key points to note:

- `select_expression` generally a vector
- `alternative_#` is a value that the vector may take on
- Compiler checks whether `select_expression == alternative_#` is true. If so, `statement_#` will be executed.
- Only statement corresponding to matching alternative will be executed
- If none of the specified items match, default statement will execute
  
# Compare and contrast hardware: case vs nested if-else



- Similar functionality is possible using the two structures
- Case structure is more “flat”, whereas if-else is more hierarchical
  - ▷ Can be an important distinction when we move to synchronous logic

## Key points to keep in mind

- Make sure the select expression and case alternatives are same length
- Can include `begin... end` to execute multiple statements within an item
- Can specify multiple case expressions separated by commas to execute the same assignment for multiple conditions:  
    `3'b001, 3'b011: a = b;`
- If multiple items match, the first will be the one that is used
  - ▷ Don't rely on this! Make sure your case items are unique!


## A second example

```
always @ *  
  case( { s2, s1, s0 } )  
    3'b010: y = d2;  
    3'b100: y = d4;  
    3'b101: y = d5;  
    3'b101: y = d0; // this will be ignored  
    3'b011: y = d3;  
    3'b000: y = d0;  
    3'b001: y = d1;  
    default: y = 1'b0;  
  endcase
```

- Synthesis translator uses a template hardware structure for the case logic
- Actual case items and assignment values are plugged into the template



# Hardware for second example

 

initial template used by translator

after translator is finished

## casex statement

- Verilog includes a variation of the case statement known as 'casex', which handles don't care values (x) in the case items.
- When the compiler sees a don't care value, it expands it out into all of the possible values before proceeding with the template matching
- Be careful - it is easy to duplicate cases and create unintentional behavior in this way.

## casex example

```
module data_selector (  
    input a, b, c, d, e,  
    input [2:0] sel,  
    output reg y );  
  
always @ *  
    casex ( sel )  
        3'b1xx: y = a;  
        3'bxx0: y = b;  
        3'b101: y = c;  
        3'b001: y = d;  
        3'b010: y = e;  
    endcase  
endmodule
```

## casex example - equivalent case statement

```
module data_selector (
    input a, b, c, d, e,
    input [2:0] sel,
    output reg y );
```

```
always @ *
    casex ( sel )
        3'b1xx:  y = a;
        3'bxx0:  y = b;
        3'b101:  y = c;
        3'b001:  y = d;
        3'b010:  y = e;
```

```
    endcase
endmodule
```

```
module data_selector (
    input a, b, c, d, e,
    input [2:0] sel,
    output reg y );
```

```
always @ *
    case ( sel )
        3'b100, 3'b101, 3'b110, 3'b111:  y = a;
        3'b000, 3'b010, 3'b100, 3'b110:  y = b;
        3'b101:  y = c;
        3'b001:  y = d;
        3'b010:  y = e;
```

```
    endcase
endmodule
```

## Danger: latch warning! (part 2)

- If you don't specify all of the possibilities for the case select variable (and don't provide a default case), the synthesis tool won't know what to connect to the corresponding input.
- As in the if-else scenario, it is possible that the compiler will add a “trivial assignment”  
`out = out;` creating feedback and the potential for a combinational latch
  - ▷ Unpredictable behavior
  - ▷ Differences between simulation and hardware
- To avoid such problems, **be sure to always include a default case!**

# Challenge

Try to write a Verilog module to solve the following problem

Generate a combinational circuit which accepts a 4-bit input called “value” and outputs a 3-bit value called “ones” which indicates the number of bits in “value” which are currently set to 1.

Thank you!  
Have a great day!