

# CME 341: Introduction to Synchronous Logic in Verilog

Brian Berscheid

Department of Electrical and Computer Engineering  
University of Saskatchewan



# Today's agenda

## 1 Introduction to Synchronous Logic in Verilog

# Introduction to Synchronous Logic in Verilog



# Synchronous logic<sup>1</sup>

- Refers to logic that operates based on a clock signal (typically at the positive edge)
- Key element is a “flip-flop” or “register”: passes signal from input to output on clock
- Generates a sequence of values which change on positive clock edges
- Note that synchronous logic generally combines flip-flops with combinational logic gates
- Quartus can infer flip-flops (FFs) using behavioral code
  - ▷ Procedures beginning with `always @ (posedge clk)`
  - ▷ The behavior that we describe will determine what FF primitive will be instantiated and what logic is built around it

---

<sup>1</sup>Also known as sequential logic


# Review: D flip-flop

  




“When the positive edge of the clock arrives, copy D to Q.”
 
# Verilog code for basic D-FF

```
reg q_posedge;  
reg q_negedge;  
  
// positive edge triggered  
always @ (posedge clk)  
    q_posedge = d;  
  
// negative edge triggered  
always @ (negedge clk)  
    q_negedge = d;
```



# D flip-flop with enable

   

“When the positive edge of the clock arrives, copy D to Q only if enable is active. Otherwise, do not update Q.”

Based on this description, try to write the Verilog code for an enabled D-FF.

## Verilog for D-FF with enable

```
reg q;

always @ (posedge clk)
  if (enable == 1'b1)
    q = d;
  else
    q = q; // optional, but recommended for clarity
           // (compiler will insert for us if we forget)
```

Note: Feedback in synchronous logic is OK! The guideline to avoid feedback applies only to purely combinational logic. Feedback loops which include registers are synchronized to a clock signal and are generally safe from instability (providing setup and hold requirements are met).



Thank you!  
Have a great day!