

# CME 341: Synchronous Logic, Part 3

Brian Berscheid

Department of Electrical and Computer Engineering  
University of Saskatchewan



# Today's agenda

- 1 Asynchronous vs synchronous loads in D-FFs
- 2 Example synchronous circuits
- 3 Synchronous logic summary


## Asynchronous vs synchronous loads in D-FFs

# Recall: asynchronous load in D-FFs

```

reg q;

 
always @ (posedge clk or posedge load)
if (load == 1'b1)
    q = load_val; // load_val is a variable
else
    q = d;
  
```



Problem: most FPGAs use FFs that only have an asynchronous clear port!  
(no asynchronous reset)
 
# Asynchronous set with only asynchronous clear


Quartus will actually build this if you ask for async set functionality



- Inverters on input and output cancel with respect to the  $D \rightarrow Q$  path
- Asserting clear “clears” the internal FF, but the observable `Q` output is “set”
 
# Asynchronous load with only asynchronous clear


Quartus will actually build this if you ask for async load functionality



- Either set or clear can trigger the clear port on the FF
- Latch circuit (bottom of diagram) used to control whether to use inverters or not
  - ▷ Latches generally undesirable... typically better to avoid asynchronous loads
  - ▷ Generally recommend using synchronous loads instead

 
## D-FFs with synchronous load

- Loads a constant or variable into a FF *on a clock edge*
- Only clock needs to go in the procedure sensitivity list
- Compiler will build logic in front of the FF to control the FF's D input to perform the load


 
# Verilog code for D-FFs with synchronous load

```
always @ (posedge clk)
  if (load_n == 1'b0)
    Q = variable_to_load;
  else
    Q = D;
```






## Example synchronous circuits
 
## Example 1: Synchronous counter with synchronous load

Design a 12-bit counter which can be synchronously loaded with the value 43.



# Synchronous counter with synchronous load: a solution


```

module my_counter (
    input wire      clk,
    input wire      load,
    output reg [11:0] count
);



always @ (posedge clk)
    if (load == 1'b1)
        count = 12'd43;
    else
        count = count + 12'd1;

endmodule

```

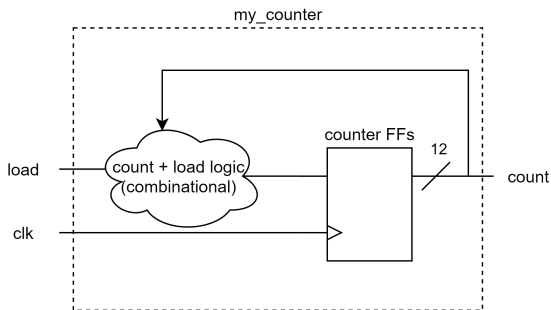

## Example 2: 3-bit ripple counter

  

## 3-bit ripple counter: a solution

```
module ripple_counter (  
    input wire clk,  
    output reg [2:0] q  
);
```

```
    always @ (posedge clk)  
        q[0] = ~q[0];  
    always @ (negedge q[0])  
        q[1] = ~q[1];  
    always @ (negedge q[1])  
        q[2] = ~q[2];
```

```
endmodule
```

## Example 3: Decimal counter

Create a counter that counts from 2 to 9 and then rolls over back to 2 and repeats.

## Decimal counter: a solution

```
module decimal_counter (  
    input  wire      clk,  
    output reg [3:0] count  
);  
  
always @ (posedge clk)  
    if (count == 4'd9)  
        count = 4'd2;  
    else  
        count = count + 4'd1;  
  
endmodule
```

What would happen if count somehow became equal to 4'd11? How could we fix this problem?

## Example 4: Ring counter

Create a 3-bit “ring counter” that generates the following sequence of outputs:  
 $001 \rightarrow 010 \rightarrow 100 \rightarrow 001 \rightarrow 010 \rightarrow \text{etc...}$

Sketch the hardware corresponding to the circuit you designed.



## Synchronous logic summary

# Synchronous logic

- The basic element of synchronous logic is the FF
- Synchronous logic is built in procedures with edge-sensitive signals in the sensitivity list:  
ie, always @ (posedge clk)
- If multiple edge-sensitive signals are in the sensitivity list, all but one must be checked in the procedure body
  - ▷ The checked signal(s) will be used for asynchronous set/clear functionality
  - ▷ The unchecked signal (one only!) will be used as the clock
- Synchronous set/clear/load functionality is built using combinational logic in front of the FFs
  - ▷ The set/clear/load trigger signal is not put in the sensitivity list in this case

# Review exercise 1: identify the hardware (A, B, or C) for each code block

A	B	C
<p>1.</p> <pre>always @(posedge clk) if (clear == 1'b1) q = 1'b1; else q = d;</pre>	<p>2.</p> <pre>always @(posedge clk or posedge clear) if (clear == 1'b1) q = 1'b0; else q = d;</pre>	
<p>3</p> <pre>always @(posedge clk or posedge load) if (load == 1'b1) q = d1; else q = d;</pre>	<p>4</p> <pre>always @* if (clear == 1'b1) q = 1'b1; else q = d;</pre>	
<p>5</p> <pre>always @(posedge clk) if (load == 1'b1) q = d1; else q = d</pre>	<p>6</p> <pre>always @* if (load == 1'b1) q = d1; else q = d;</pre>	

# Review exercise 2: identify the properties of each code block

Please check the appropriate boxes with a ✓

	Has feedback from output to input	Could be in front of D input in DFF	Could use the enable input on DFF	Use DFF with set/clear inputs
<pre>always @(posedge clk) if (time == 3'b010)   data = data_path-1 else   data = data_path-2</pre>				
<pre>always @(posedge clk or posedge clear) if (clear == 1) counter = 8'b0; else if (set == 1)   counter = 8'hFF; else   counter =     counter + 8'h01;</pre>				
<pre>always @(posedge clk or posedge load) if (load == 1'b1) timer = 16'd5760; else if (pause == 1'b1)   timer = timer; else   timer =     timer - 16'd1;</pre>				
<pre>always @(posedge clk) case (s); 2'd0: state = state-2; 2'd1: state = state; 2'd2: state = state-1; 2'd3: state = 6'h37; end case</pre>				

Thank you!  
Have a great day!