

# CME 341: Logic Mapping for Relational Operators

Brian Berscheid

Department of Electrical and Computer Engineering  
University of Saskatchewan



# Today's agenda

## 1 Logic Mapping for Relational Operators

## Logic Mapping for Relational Operators

## Relational operators: review

- As discussed previously, relational operators compare two input vectors and produce a single output bit (1 if the comparison is true, 0 if false)
- List of relational operators:
  - ▷  $<$  less than
  - ▷  $<=$  less than or equal to
  - ▷  $>$  greater than
  - ▷  $>=$  greater than or equal to
  - ▷  $==$  equal to
  - ▷  $!=$  not equal to
- Often used to generate select signals for if-else constructs
- Key question for today: *What type of hardware structure is generated by each?*


## Logic for $A == B$

- For two numbers to be equal, all of their individual bits must match ( $A[0] == B[0]$ ,  $A[1] == B[1]$ , etc.)
- Two bits can be compared using an XNOR gate (XNOR generates 1 if bits match)

A[i]	B[i]	A[i] XNOR B[i]
0	0	1
0	1	0
1	0	0
1	1	1

- Combine results of XNORs together using AND gate to generate final output  $A == B$

# Hardware structure for $A == B$

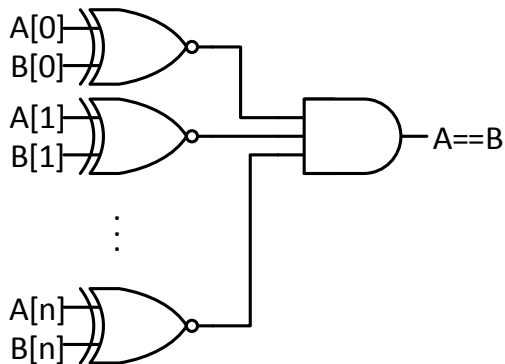


# Simple always procedure using ==

Sketch the hardware generated by this code

```
input [3:0] a, b;
output [3:0] c;
reg [3:0] c; // The output of a procedure must be declared type reg


always @ (*)
begin // begin-end are unnecessary if procedure has a single statement
    if(a == b)
        c = 4'b1011;
    else
        c = 4'b0011;
end
```

# Recall: if-else template

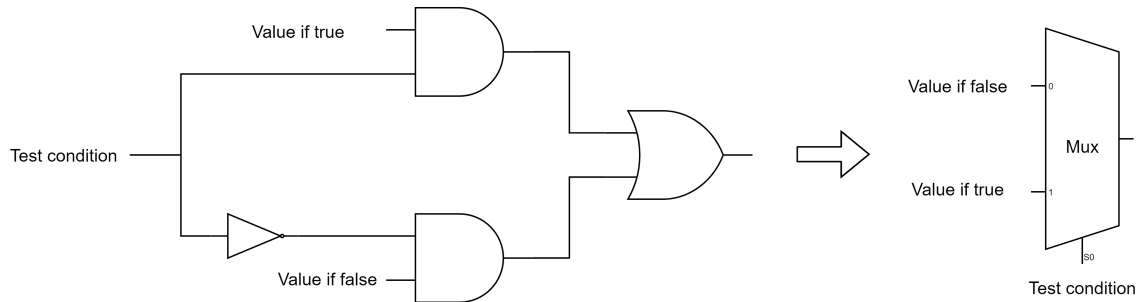




# Template applied to procedure:

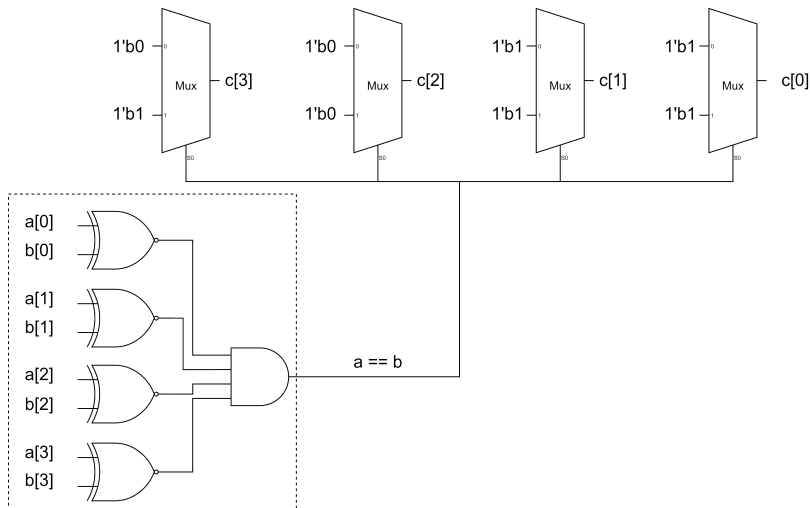
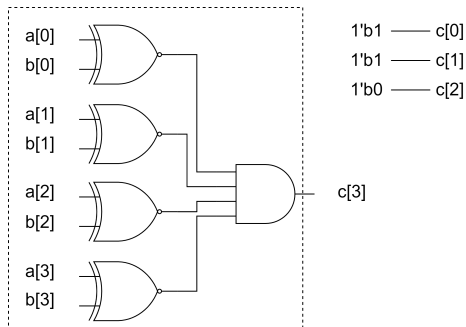
# Quartus optimizer removes unnecessary logic... final circuit built in FPGA



# Not equal to operator ( $\neq$ )


- This is trivial once we know how to do the equal to operator
- Just build the equal to logic, then invert the result
- Nothing more to be said...

# Greater than operator ( $>$ )

(For unsigned numbers, different for signed case)


- Algorithm to check if  $A > B$ 
  - ▷ Compare MSBs of A and B
    - If MSB of A = 1 and MSB of B = 0,  $A > B$  is true ... stop!
    - If MSBs are the same, continue...
  - ▷ MSBs are same, so compare 2nd MSB of A and B
    - If 2nd MSB of A = 1 and 2nd MSB of B = 0,  $A > B$  is true ... stop!
    - If 2nd MSBs are the same, continue...
  - ▷ First 2 MSBs are same, so compare 3rd MSB of A and B
  - ▷ Etc...
  - ▷ All but LSBs are same, so compare LSB of A and B
    - If LSB of A = 1 and LSB of B = 0,  $A > B$  is true ... stop!
    - Otherwise,  $A > B$  is false!
    - Note that if we reached this point and LSBs are the same,  $A == B$
- (Not complicated... this is just how we compare numbers in our everyday lives!)

# Hardware for $>$ operator

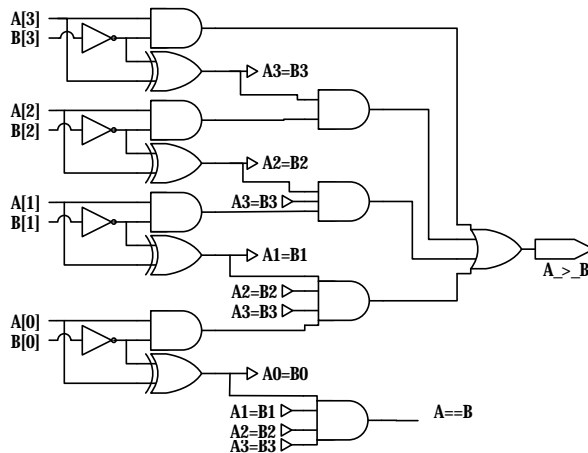
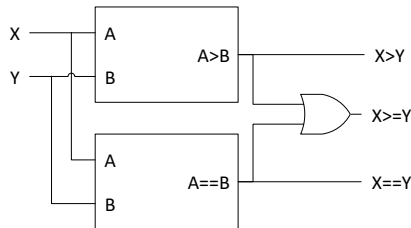
## Remaining relational operators are simple!

- $A \geq B$  ... just OR the  $A > B$  and  $A == B$  outputs from the previous slide
- $A < B$  : equivalent to  $B > A$  ... just switch the places of A and B in previous slide
- $A \leq B$  ... just OR  $A < B$  with  $A == B$
- Template for all relational operators:



Thank you!  
Have a great day!