

# CME 341: Latches and Flip-flops

Brian Berscheid

Department of Electrical and Computer Engineering  
University of Saskatchewan



# Today's agenda

## 1 Review of Latches and Flip-flops


## Review of Latches and Flip-flops

# Latches and Flip-flops

- Latches and flip-flops are circuits that can store state information in a digital circuit
- Latches are not clocked, but can be used to create flip-flops (which are clocked)
- Some examples and early assignment questions in CME 341 involve latches
- Latches can be dangerous and generally shouldn't be used in actual designs in CME 341 (or ever)
  - ▷ 99.9% of the time, you really want a flip-flop
  - ▷ Quartus will sometimes generate latches if you use incorrect coding styles; we will study how to avoid this later

 
# Set-clear latch

Practice: Try to generate a truth table for this circuit




# Verilog code for the s-c latch

Try to write it yourself before peeking

 

# Verilog code for the s-c latch


Try to write it yourself before peeking

 

```
module set_clear_latch (  
    input wire n_set,  
    input wire n_clear,  
    output wire Q,  
    output wire n_Q  
);  
  
    assign Q    = ~(n_set & n_Q);  
    assign n_Q = ~(n_clear & Q);  
  
endmodule
```
 
# Transparent latch


Practice: Try to generate a truth table for this circuit






# Verilog code for the transparent latch

Try to write it yourself before peeking

 

# Verilog code for the transparent latch

 

```
module transparent_latch(D, Gate, Q);
input D, Gate;
output Q;
```

```
wire D_bar, set_bar, clear_bar;
```


```
assign set_bar = ~(D & Gate);
assign clear_bar = ~((~D) & Gate);
```

```
set_clear_latch latch_1(.n_set(set_bar),
.n_clear(clear_bar),
.Q(Q)); // n_Q output not used
```

```
endmodule
```

# A D-flip-flop can be built from transparent latches

Positive edge-triggered logic

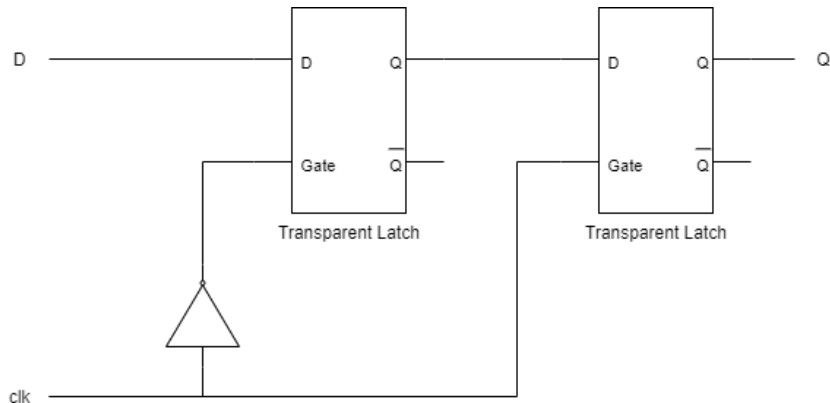

Thank you!  
Have a great day!