

CME 341: Blocking vs Non-blocking Assignments

Brian Berscheid

Department of Electrical and Computer Engineering
University of Saskatchewan



Today's agenda

1 Verilog assignment operators overview

Verilog assignment operators overview

Verilog assignment operators

- Up to this point in CME 341, we have used the `=` operator to perform assignments
- In fact, there are two distinct assignment operators in Verilog
 - ▷ The blocking assignment operator (`=`)
 - ▷ The non-blocking assignment operator (`<=`)
- The two operators behave differently in only one specific case:
 - ▷ Synchronous procedures with `begin ... end` wrappers
- Mixing up the assignment operators can result in synthesizing unexpected hardware
 - ▷ This is a common source of bugs in CME 341 and beyond!
- Follow the synthesizable coding guidelines presented earlier to avoid this problem!

Blocking vs nonblocking: overview example

Blocking assignments

```
always @ (posedge clk)
begin
    reg_1 = in_1 ^ in_2;
    reg_2 = reg_1 & in_3;
end
```

“At each positive clock edge, load reg_1 with the XOR of in_1 and in_2. Then, compute the AND of that result and in_3. Load the result into reg_2.”


Non-blocking assignments

```
always @ (posedge clk)
begin
    reg_1 <= in_1 ^ in_2;
    reg_2 <= reg_1 & in_3;
end
```


“At each positive clock edge, compute the XOR of in_1 and in_2. Then, compute the AND of the previous value of reg_1 (prior to the clock arriving) and in_3. Assign the results to reg_1 and reg_2.”

Blocking vs nonblocking: overview example (synthesized hardware)
 
```
always @ (posedge clk)
begin
    reg_1 = in_1 ^ in_2;
    reg_2 = reg_1 & in_3;
end
```


 
```
always @ (posedge clk)
begin
    reg_1 <= in_1 ^ in_2;
    reg_2 <= reg_1 & in_3;
end
```



Blocking vs nonblocking assignment operators

- When used within a `begin ... end` block of code:
 - ▷ Blocking operator (`=`): as soon as an assignment is seen, evaluate the RHS and assign to LHS before moving to next line of code in the block


Similarity to a sequential programming language; updates “as-if” they are updated in order listed in code

Don’t forget that all FFs are updated simultaneously in parallel!
 - ▷ Non-blocking operator (`<=`): when an assignment is seen, evaluate the RHS but don’t assign the result to the LHS until the end of the code block


All assignments take effect at end of code block
- For combinational logic, the synthesized hardware will be identical
- For synchronous logic, the synthesized hardware could be different
 - ▷ Specifically, if a LHS is reused in a RHS in the same code block

Order of statements matters in a blocking assignment

HW #1

 

HW #2

 

```
always @ (posedge clk)
begin
    reg_1 = d;
    reg_2 = reg_1;
end // builds HW #1
```


```
always @ (posedge clk)
begin
    reg_2 = reg_1;
    reg_1 = d;
end // builds HW #2

always @ (posedge clk)
begin
    reg_1 <= d;
    reg_2 <= reg_1;
end // builds HW #2


always @ (posedge clk)
begin
    reg_2 <= d;
    reg_1 <= reg_1;
end // builds HW #2
```


Hardware to code example

 Write both blocking and non-blocking code to implement this hardware



 Hardware to code example: non-blocking code




```

always @ (posedge clk)
begin
    q1 <= x1 & q2;
    q2 <= (x1 & q2) | x2;
    q3 <= ((x1 & q2) | x2) ^ q2;
end

```

Hardware to code example: blocking code

 

```
always @ (posedge clk)
begin
    q1 = x1 & q2;
    temp = q2;
    q2 = q1 | x2;
    q3 = temp ^ q2;
end
// OR
```

```
always @ (posedge clk)
begin
    q1 = x1 & q2;
    q3 = (q1 | x2) ^ q2
    q2 = q1 | x2;
end
```

Final thoughts

- Blocking assignments function more like sequential programming (but still build parallel hardware)
- Non-blocking assignments perhaps more accurately reflect to the actual hardware that is being constructed
- More examples are available in the Chapter 3 part 2 notes (handwritten)
- Overall, don't stress too much about this topic. You won't run into problems as long as you follow the CME 341 coding style recommendations:
 - ▷ Avoid `begin ... end` wrappers
 - ▷ Assign one variable per `always` block
- If `begin ... end` is used in (synthesizable code), the non-blocking operator is recommended
 - ▷ Note continuous assignments (`assign a = b`), **MUST** use the blocking operator.

Thank you!
Have a great day!