FSM State Diagram of an Up−Down Counter that Pauses in State 8